

1

2

3

4


5

6


7

8


Voltage Regulators

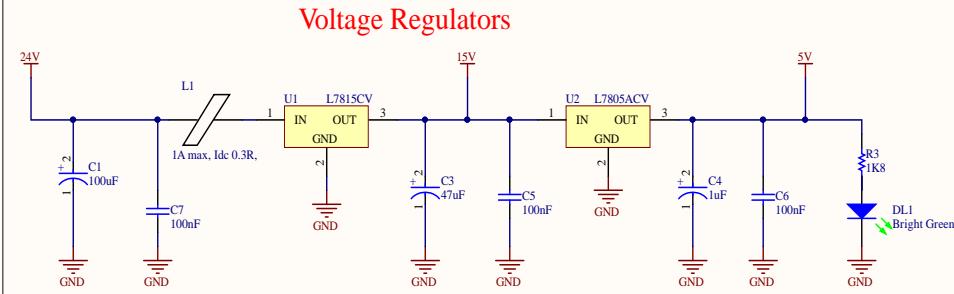


Low Pass Filter

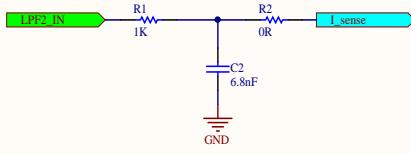


Low Pass Filter

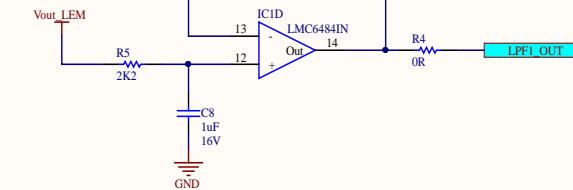


Slope Compensation Buffer 1

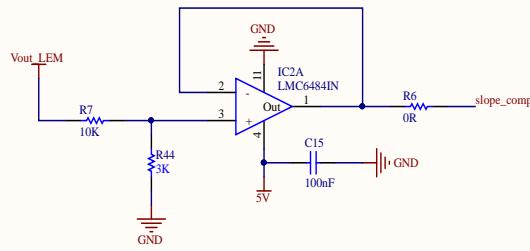


Brake Debouncing Schmitt Trigger

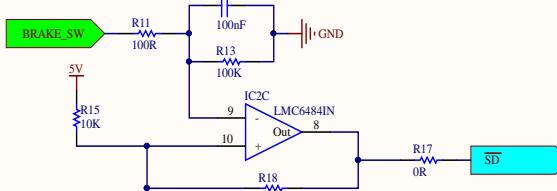


Slope Compensation Op Amp

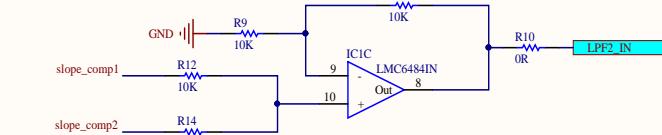


Slope Compensation Buffer 2

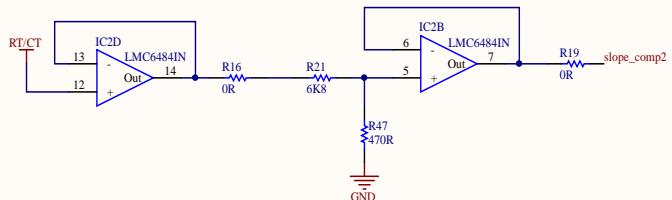


Current Mode Controller

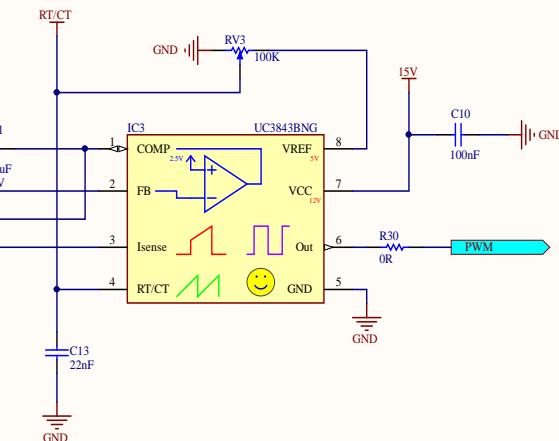


PWM Inverter

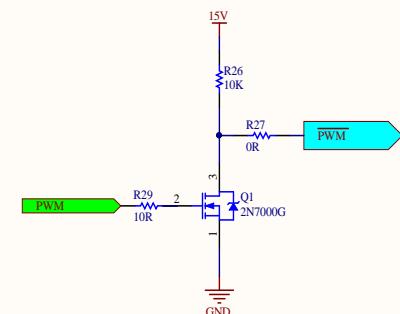


PI Controller

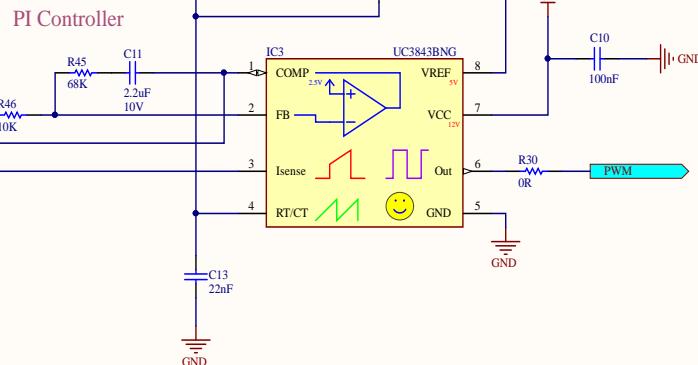



Voltage Attenuation Op Amp

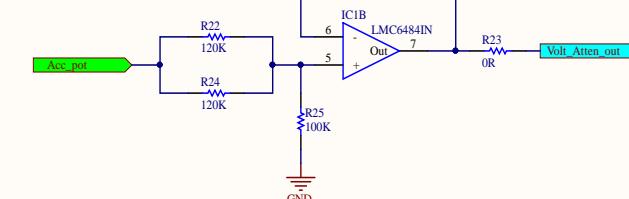

Summing Differential Amplifier

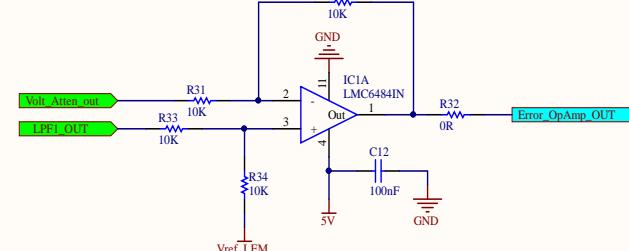

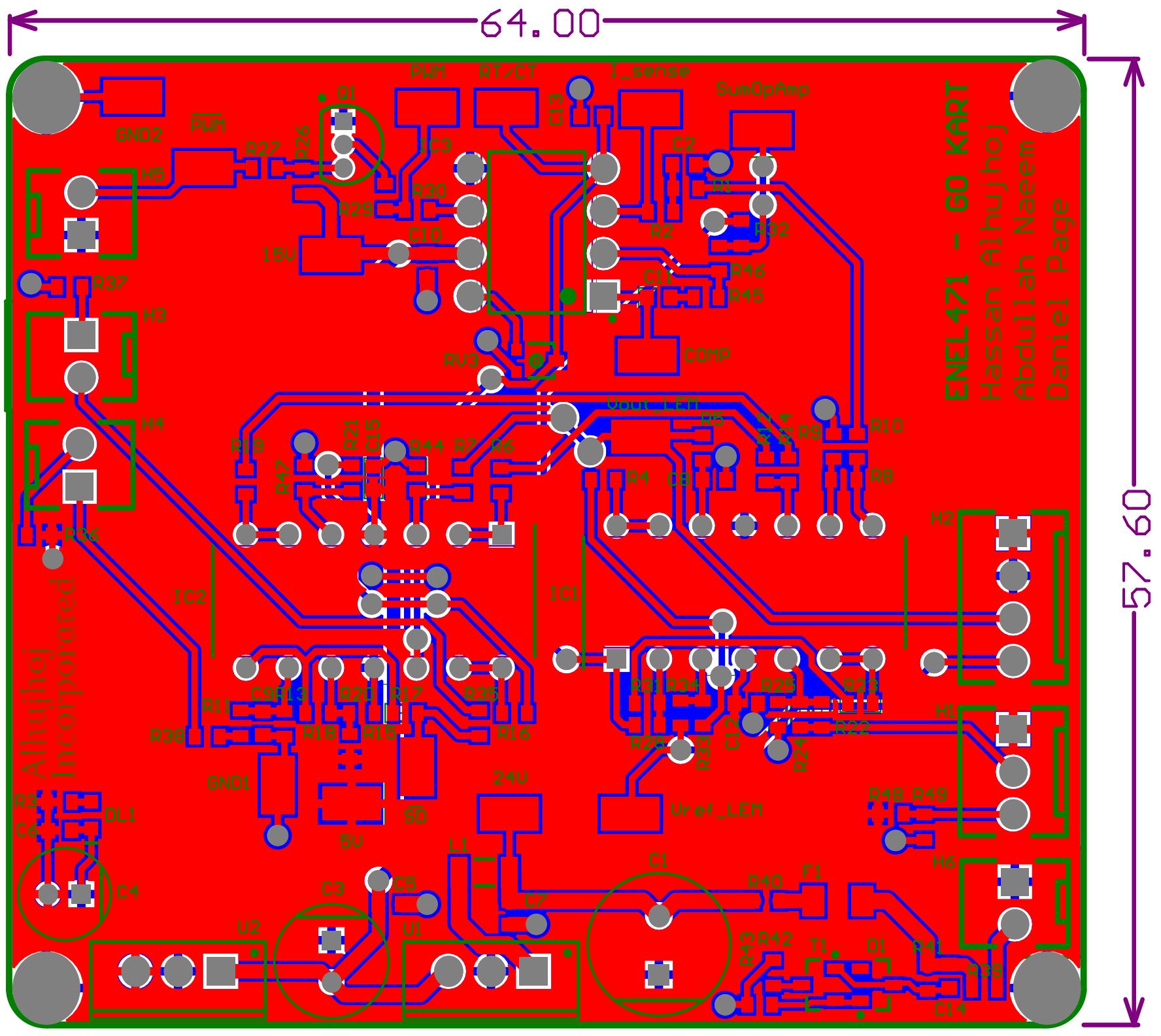

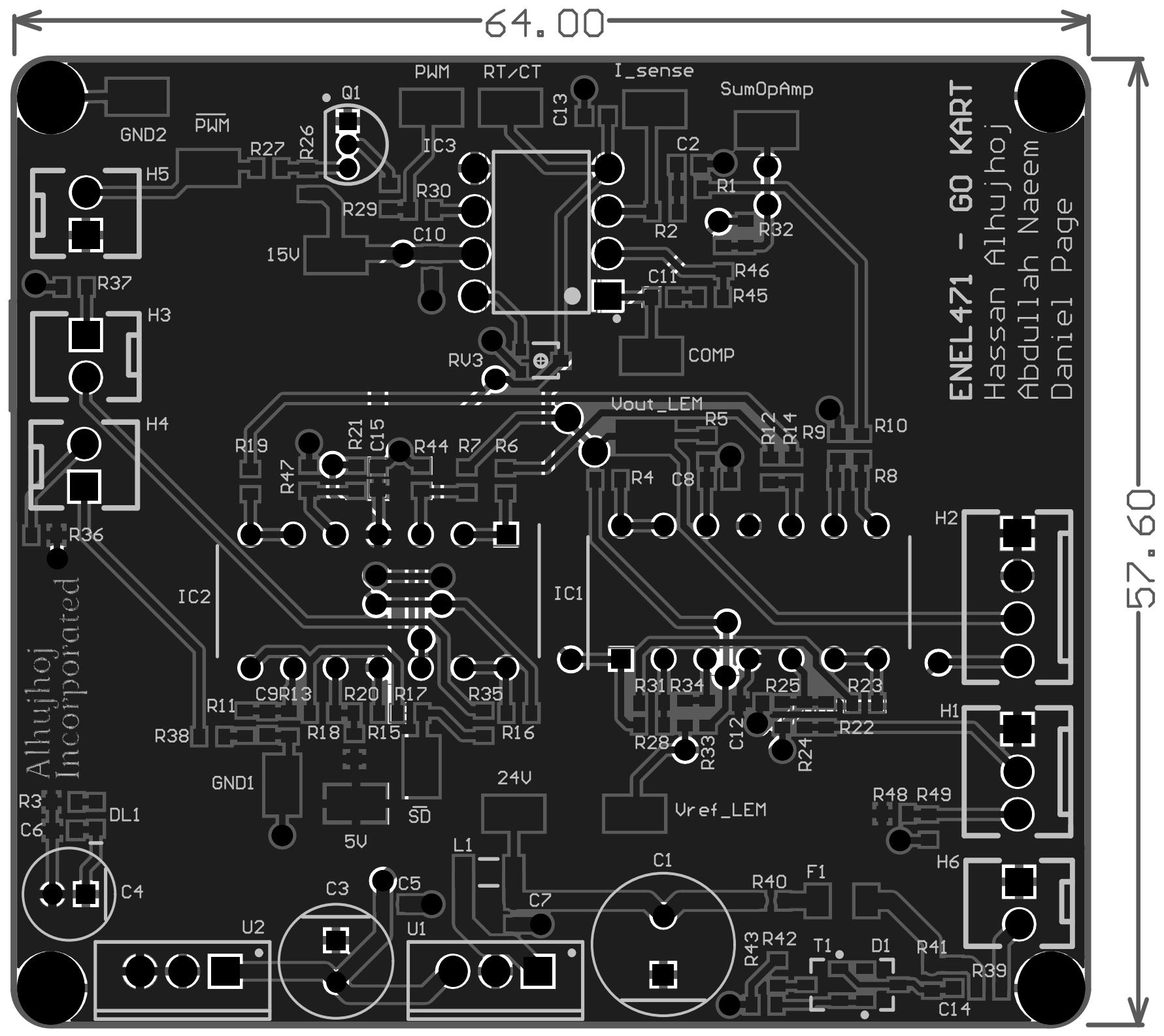

Board Slack Report

